

DLD Lab Final

CSE 2106


Marks: 20

Duration: 1 Hour 15 Minutes

Q1. [10 Marks]

Following is a State Diagram. Design the state diagram using **JK** Flip-Flops.

[Here Y = Last digit of your ID]

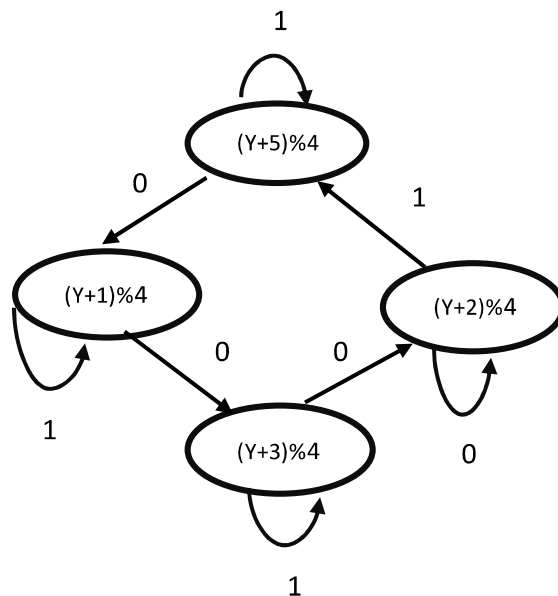

i.e.: If your ID is 14.02.04.066 then $(Y+1) \% 4 = 7\%4 = 3$

Q2. [5 Marks]

Design a **4-bit** Johnson Counter. The type of Johnson Counter (Up/Down) and type of Flip-Flop depends on your ID.

- Johnson Up counter using T Flip-Flop if ***[Last digit of your ID] % 4 = 0***
- Johnson Up counter using D Flip-Flop if ***[Last digit of your ID] % 4 = 1***
- Johnson Down counter using T Flip-Flop if ***[Last digit of your ID] % 4 = 2***
- Johnson Down counter using D Flip-Flop if ***[Last digit of your ID] % 4 = 3***

i.e.: If your ID is 14.02.04.066 then $(6\%4) = 2$ (You need to implement Johnson Down counter using T Flip-Flop)

Q3. [2.5 + 2.5 = 5 Marks]

$$F(A,B,C,D) = M_{12} \cdot M_{13} \cdot M_{15} \cdot M(x) \cdot M(x+1) \cdot M(x-1) \cdot M(x-2)$$

Implement the aforementioned expression using **DEMUX** and **MUX**.

Show all the necessary steps and draw the circuit diagram.

Here $x = [\text{last digit of your ID} \% 9] + 2$

i.e.: If your ID is 14.02.04.066 then $(x+1) \% 4 = 7\%4 = 3$

For Question **1 & 2**, you need to Design the following:

- State Diagram
- State Table
- Excitation Table
- K-Map
- Expression
- Circuit