

MID-FINAL (CSE2106)

Time: 35 min, Marks -10

Set- EVEN_ID

Consider a 4-bit binary input (**A, B, C** and **D**). There are 2 outputs (**W1** and **W2**).

If the rightmost 2 bits in the input number are greater than the leftmost 2 bits, then W1 is 1; Else W1 is 0

If the leftmost 2 bits in the input number are greater than the rightmost 2 bits, then W2 is 1; Else W2 is 0.

If the leftmost 2 bits in the input number are equal to the rightmost 2 bits, then both W1 and W2 are 0.

Submission Procedure:

- Report (PDF File) – [5]
 - Truth table
 - K-map
 - Output functions
 - Circuit diagram
- Proteus implementation (.pdsprj File) –[5]